Smart Bookstand


Project Design

Ideas behind the "Smart Bookstand"


"Your reading experience should be more than a simple woodblock"

"No bookstand has a decent lighting system embedded within"


"Why can't bookstands be portable?"

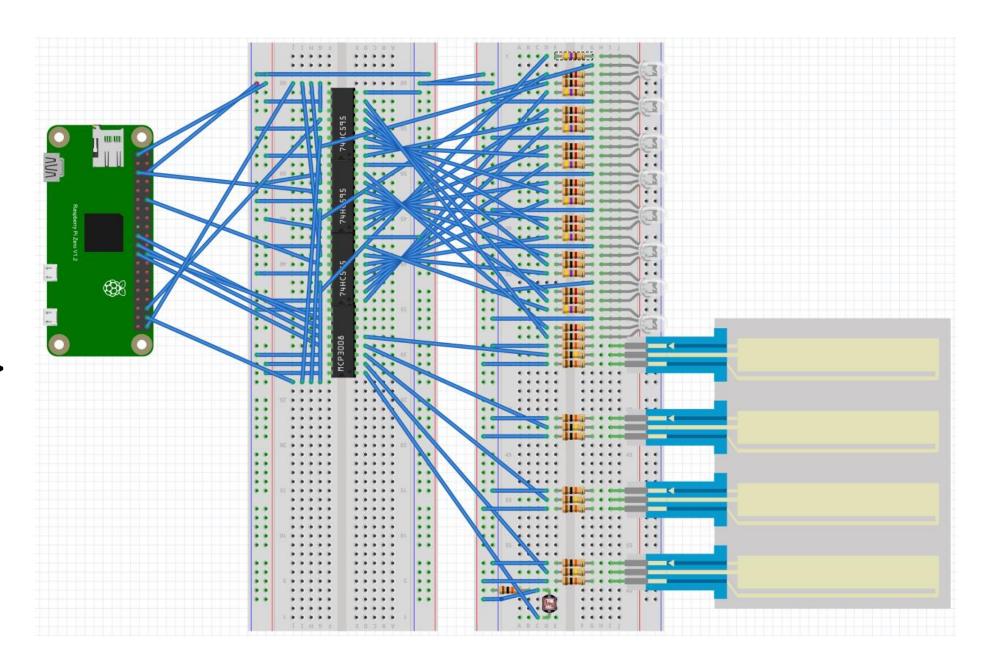


Overview <KiCAD>

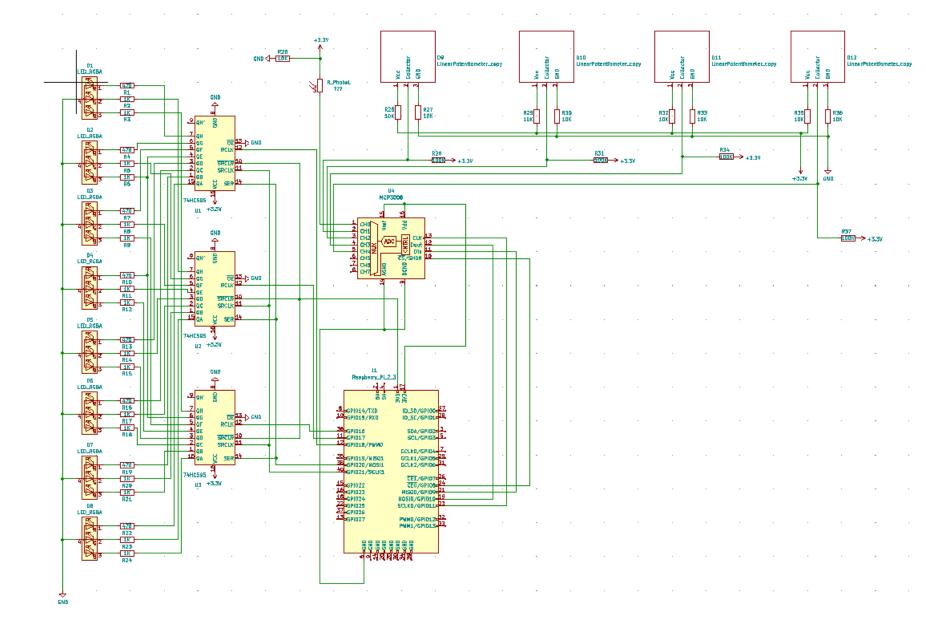


Overview KiCAD PCB Design

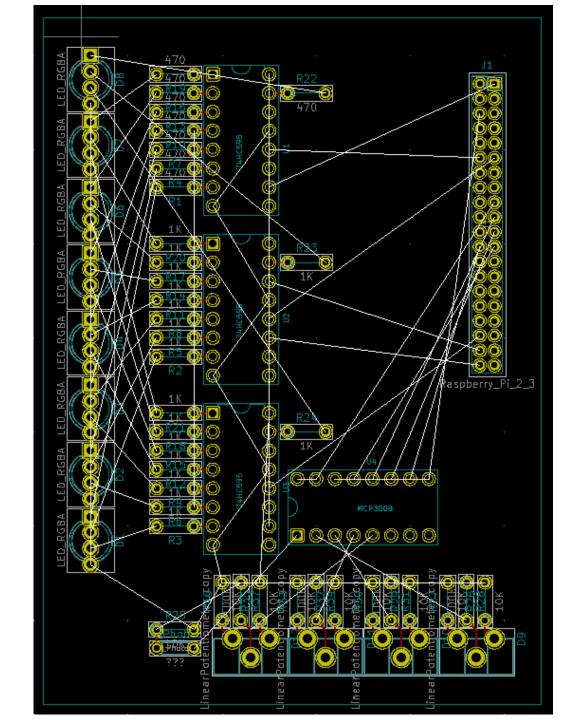


Lighting system - Fritzing

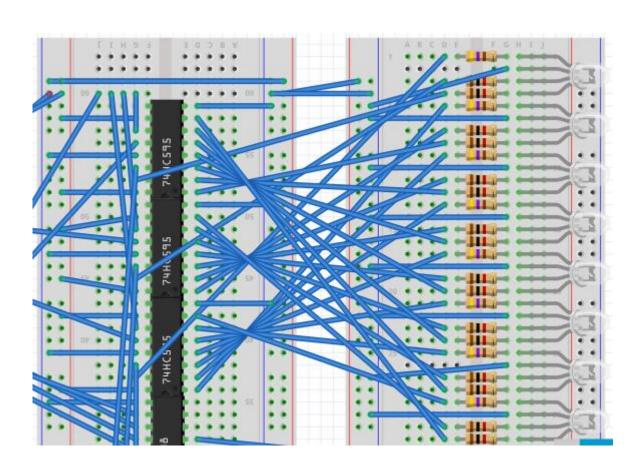

RGB LEDs – 8 of them

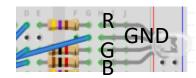

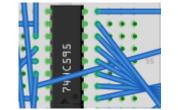
- Each with a current limiting resistor
- Red -> connected using 470Ω
- Green / Blue -> 1kΩ74HC595 Shift Register




- One for each color 3 total
- 8 outputs connected to each LED
- Will be connected to SPI1, 3CEs

I know its dizzy – Let's go into the details

Lighting system - KiCAD

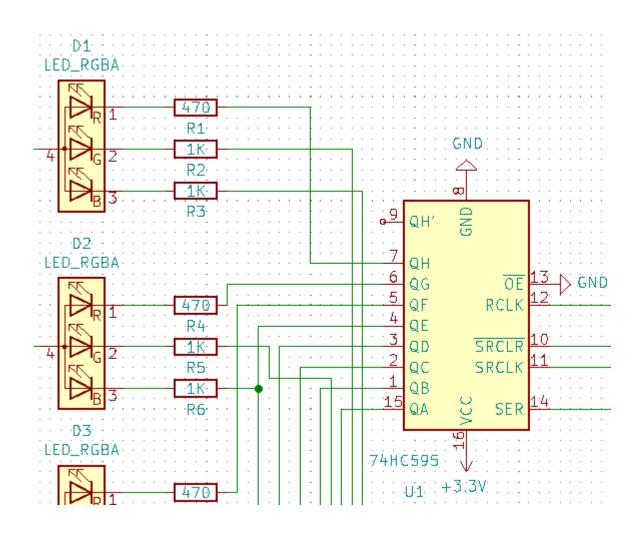

Lighting System KiCAD PCB Design

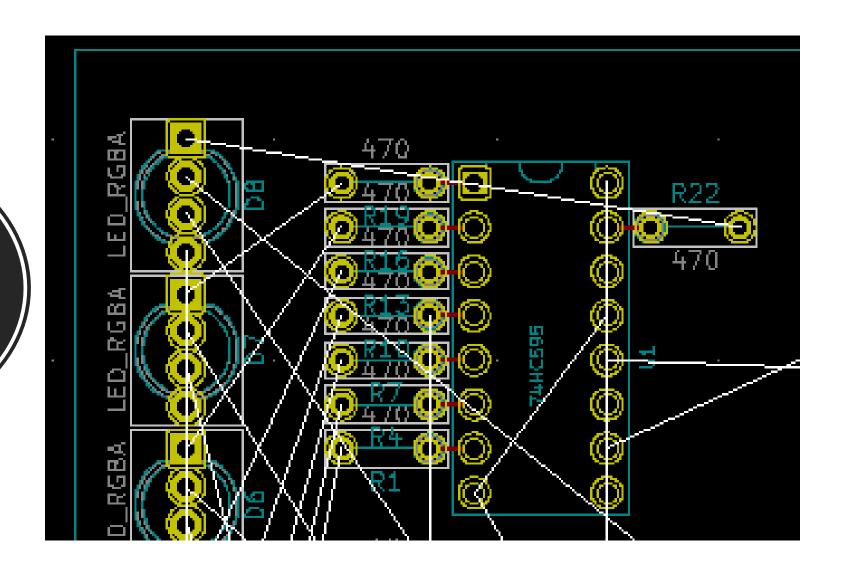


Photoresistor - Fritzing

Resistor value changes as the incoming light level varies.


Pull down resistor of $10k\Omega$


Connected to channel 0 of MCP3008


- MCP3008 operates through SPI0

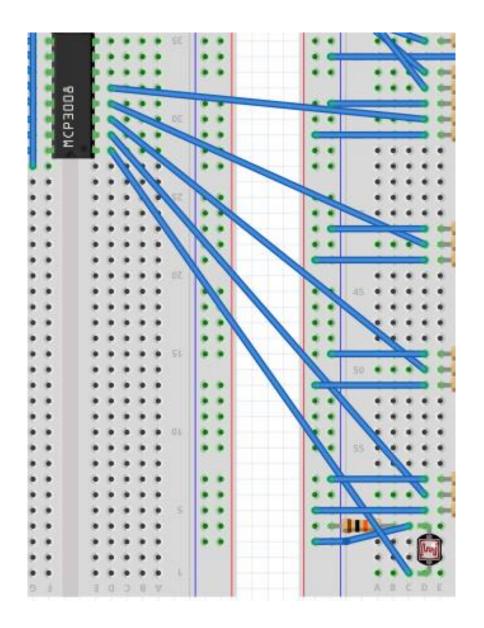

Photoresistor - KiCAD

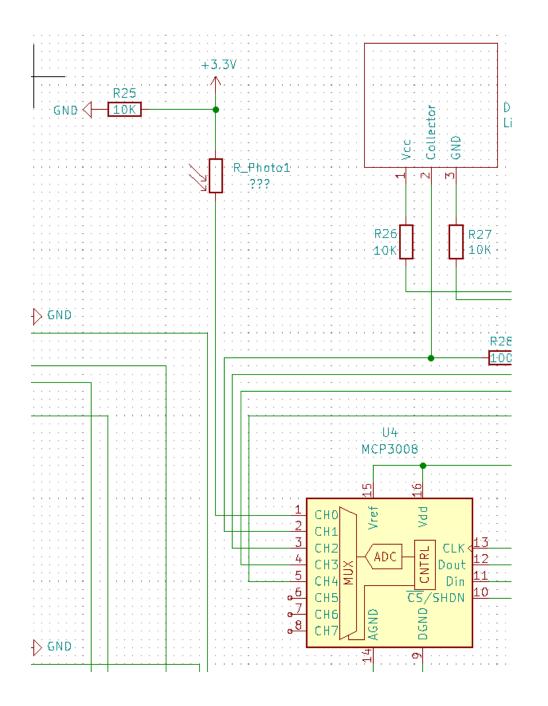

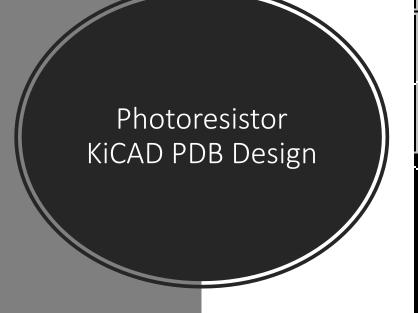


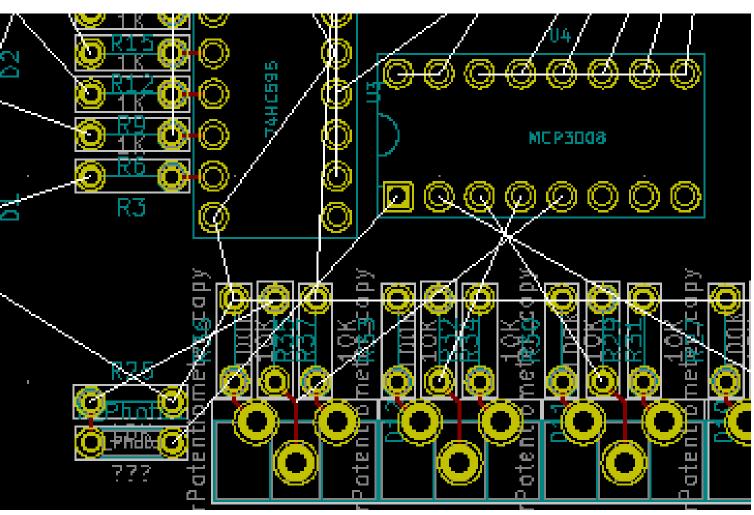

Linear Potentiometer - Fritzing

A varying resistor:

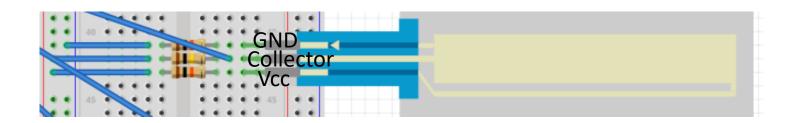
- Depending on where you touch
- Using current limiting resistors 10k on Vcc and GND
- 100k as a pullup resistor on Collector
- Closer to the collector, the smaller the resistor value
- 4 in total Connected to channel 1-4 of MCP3008




Fritzing diagram taken from following: https://github.com/sparkfun/Fritzing_Parts/blob/master/products/08680_softpot_membrane_potentiometer_50mm.fzpz

Linear Potentiometer - KiCAD



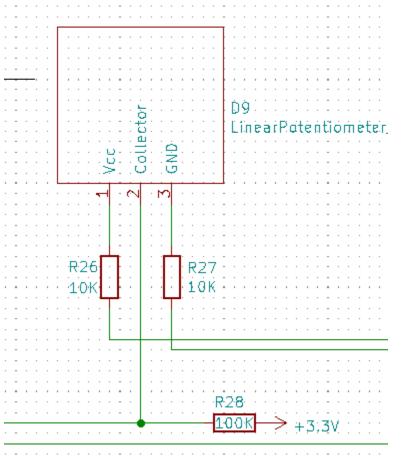

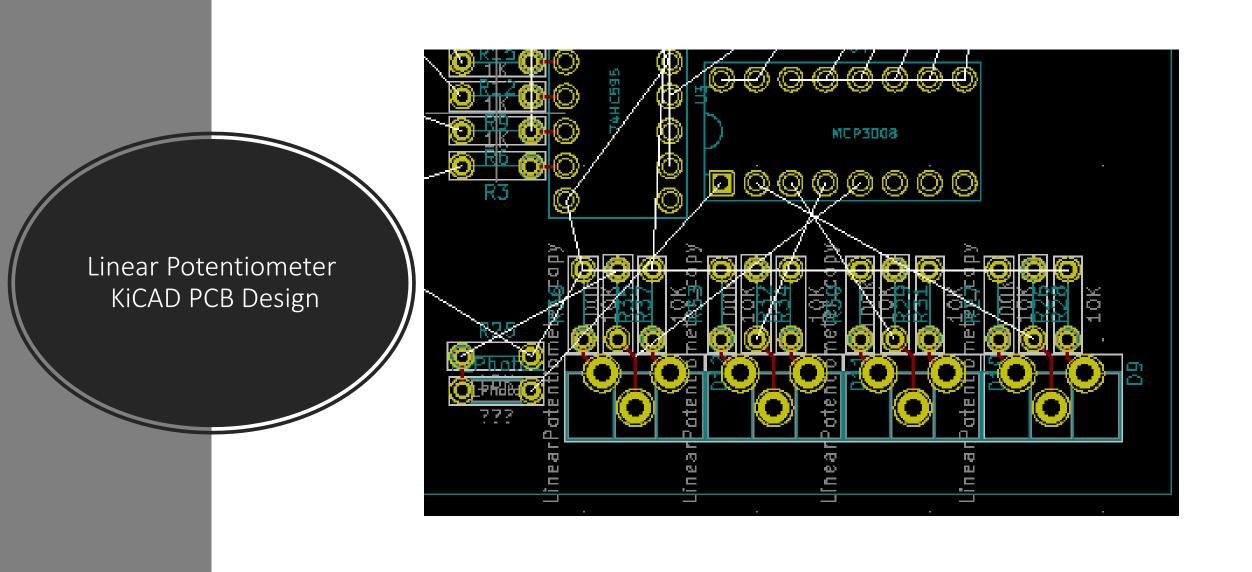

Thank you

End of Document